

ICS 4111: Embedded Systems & IoT

Practical Exercise 3: Embedded System Design

169962- Abdalla Muhammad Murshid

169004- Mohammed Ilhan Hamud.

159540- Wanjohi Joy Wambui.

156740- Gitonga Benson Kamau.

150851- Ndeti Melissa Mwende.

154210- Elvis Wafuke Wanyama.

Experiment 1

Question 1 – Resistor Identification (Colour Code)


Figure 1: Selected resistor and colour code



Resistance Value- **200 Ohms.**

Question 2 – Resistance Measurement (Multimeter)

Figure 2: Multimeter measuring resistor value

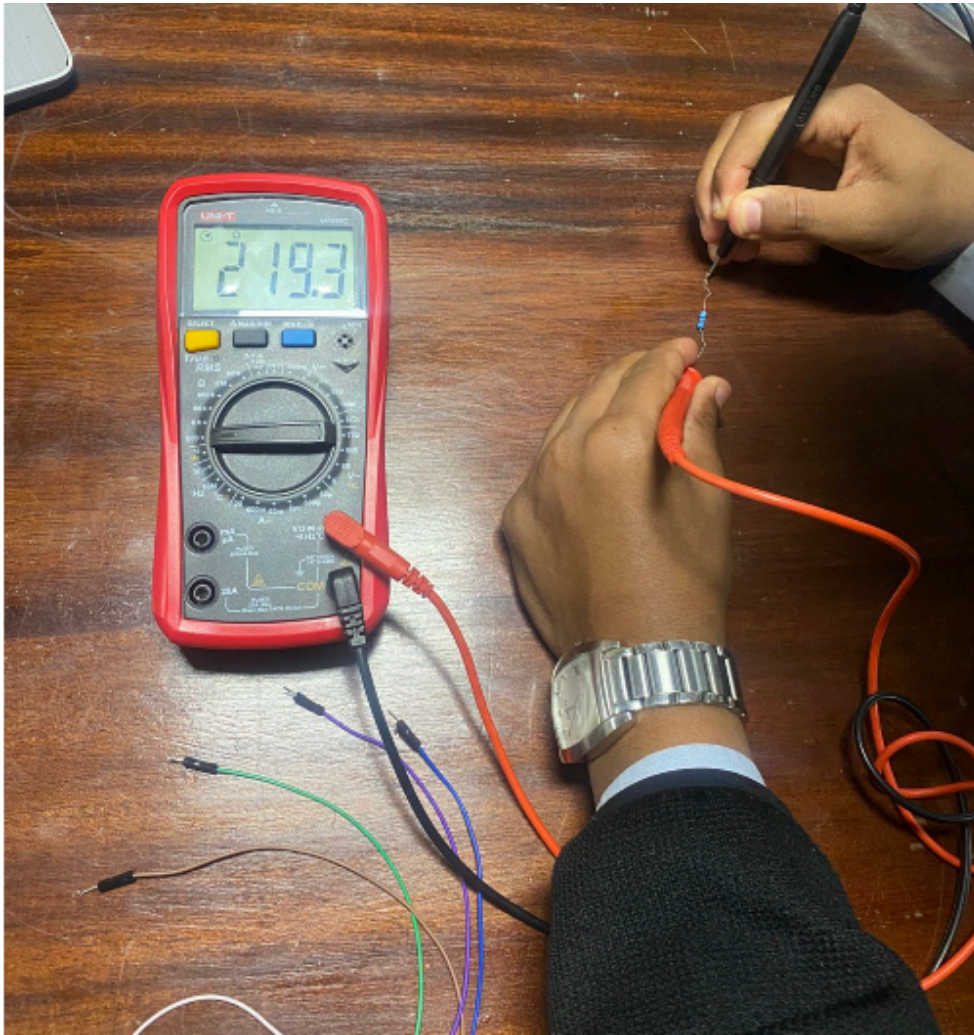


Measured Resistance: **219.3 Ohms.**

Experiment 2

Question 1 – Circuit Setup

Figure 3: Physical circuit implementation — Arduino UNO + LED

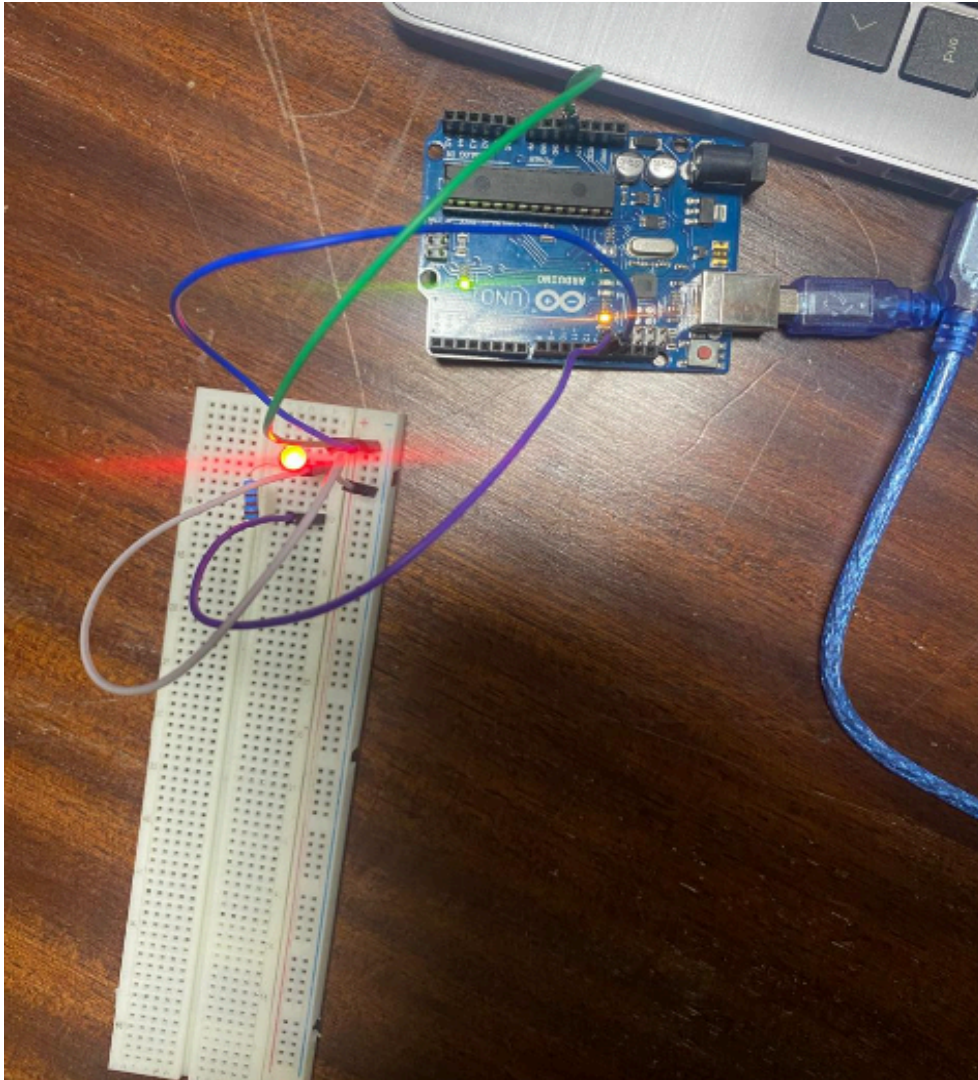


Question 2 - Code

```
void setup() {  
    pinMode(13, OUTPUT);  
}  
  
void loop() {  
    digitalWrite(6, HIGH); // LED on  
    delay(1000);  
    digitalWrite(6, LOW);  // LED off  
    delay(1000);  
}
```


Question 3 – Voltage Measurement

Figure 4: Multimeter measuring voltage across the circuit

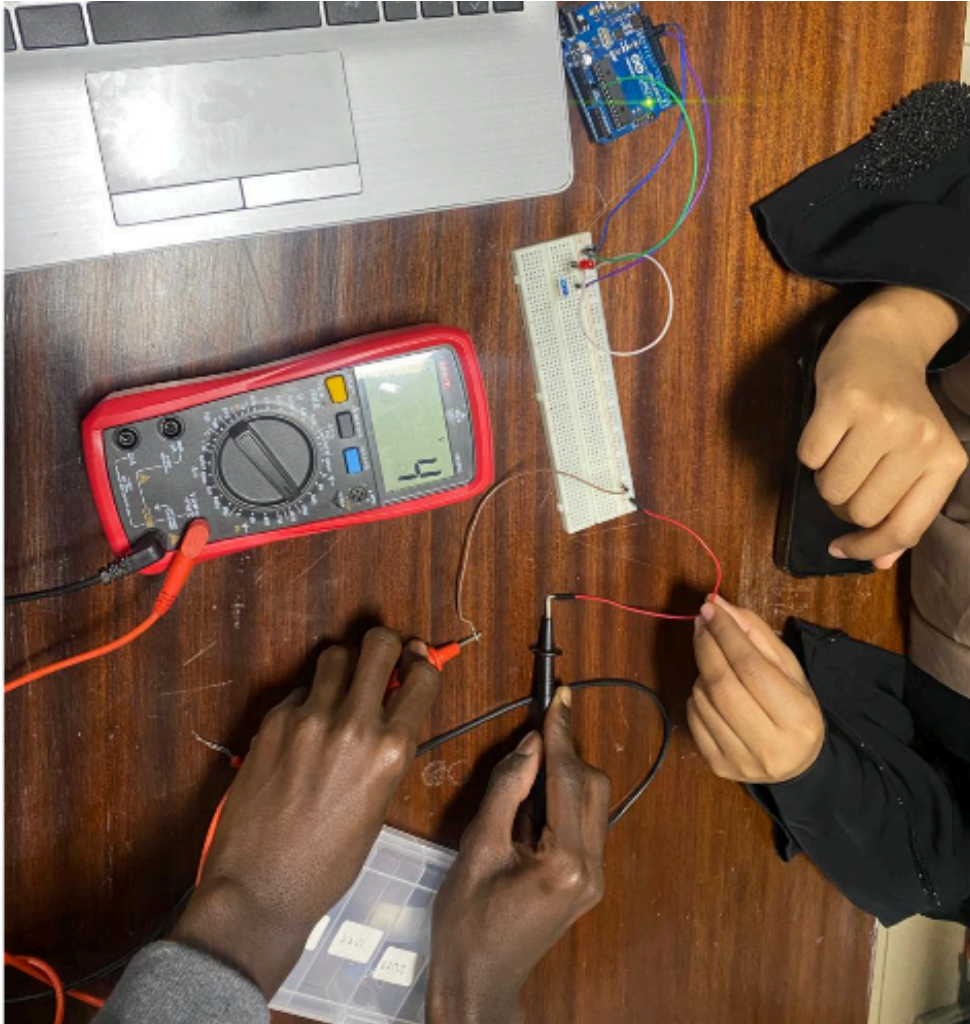

Multimeter Value: 4V

Question 4 – PWM Brightness Control (Potentiometer)

Figure 5: LED at 25% brightness

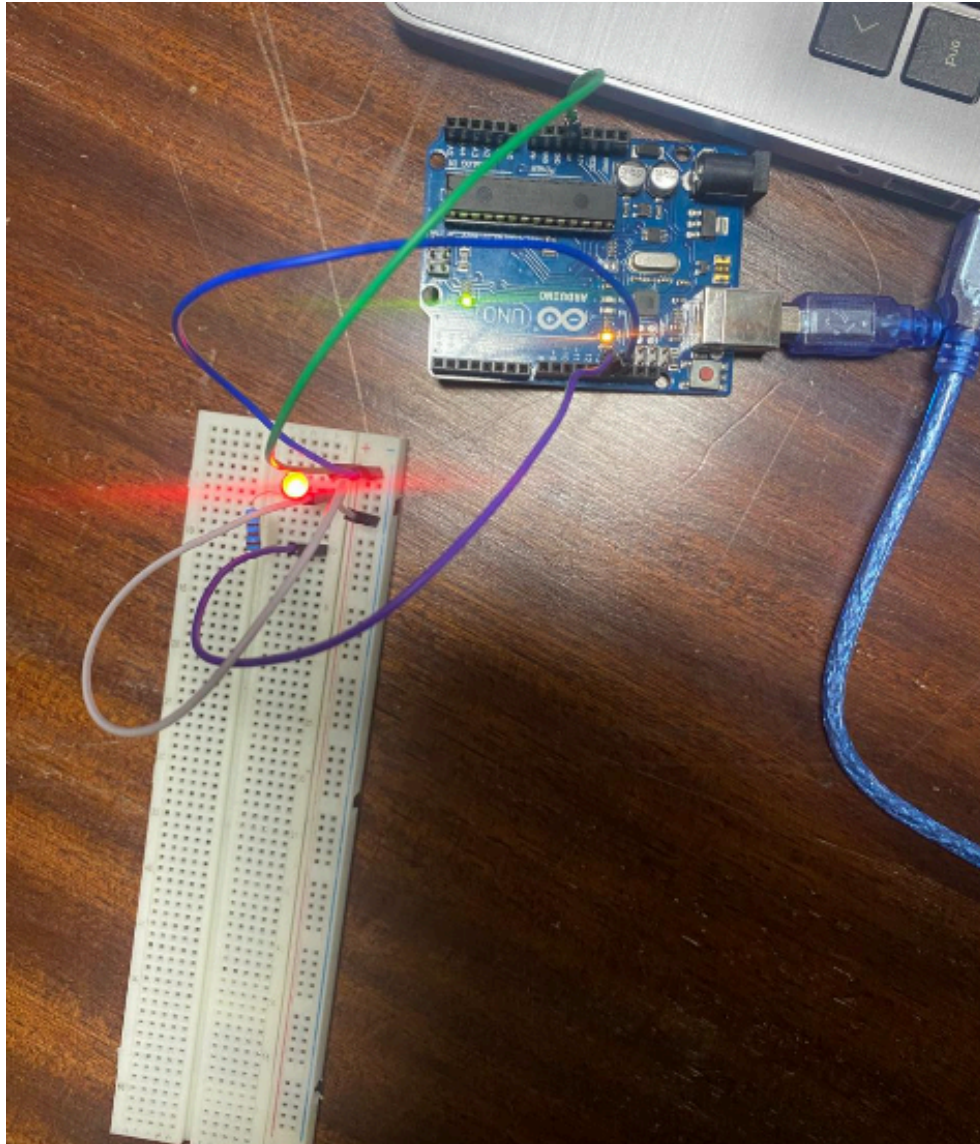


Figure 6: LED at 50% brightness


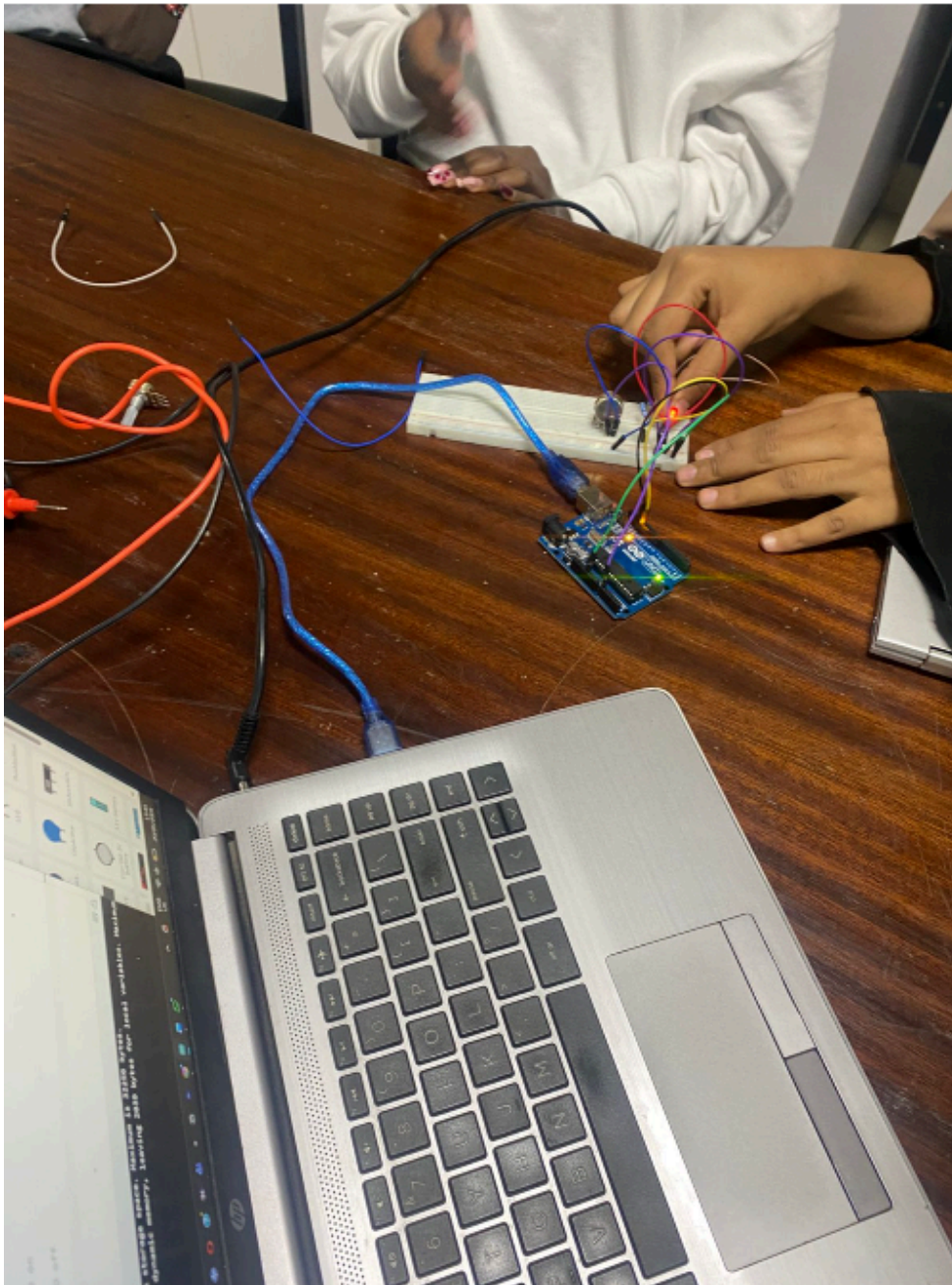



Figure 7: LED at 100% brightness

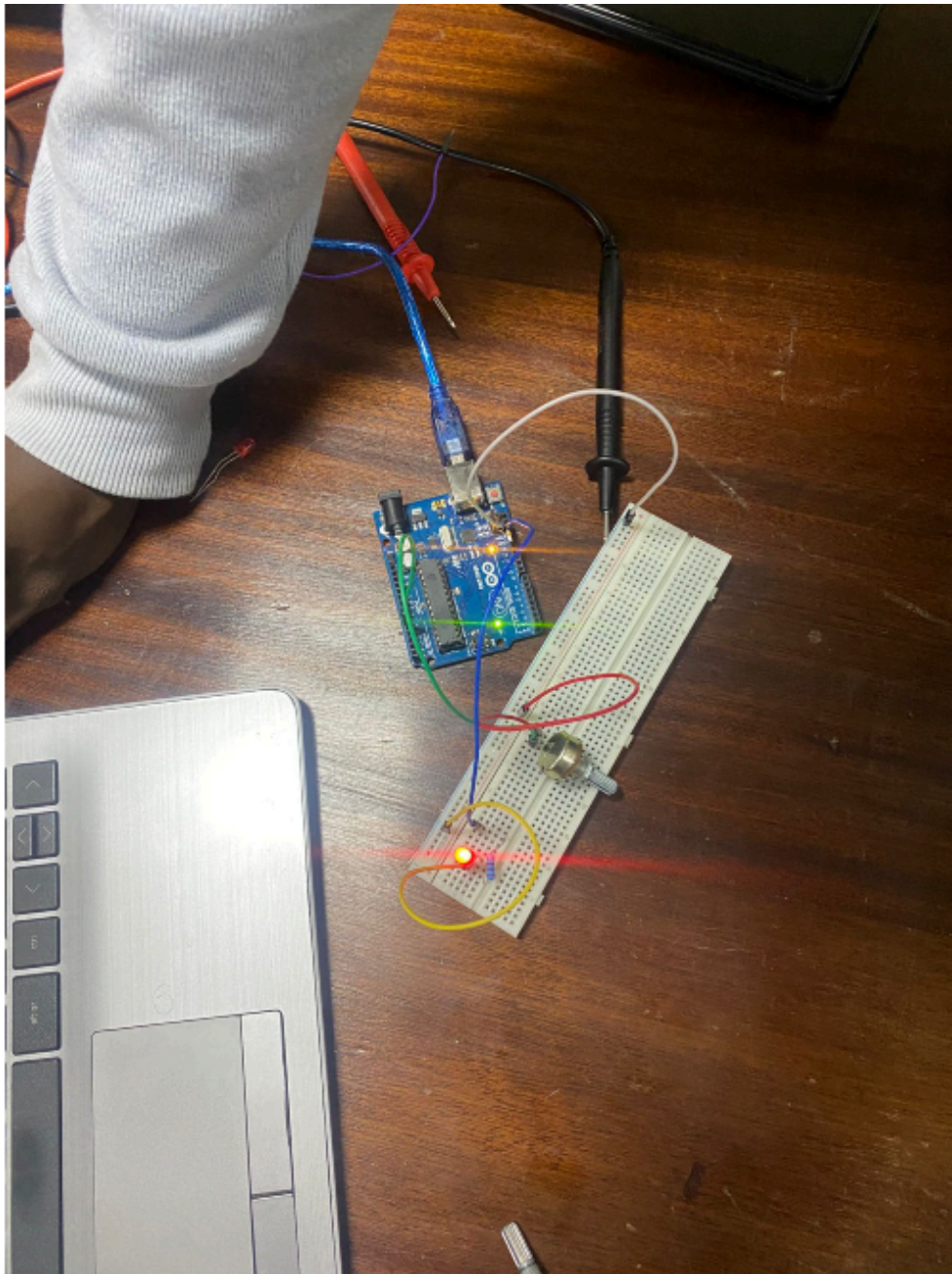

Experiment 3


Question 1 – Series Resistor Circuit

Figure 8: Physical circuit resistors connected in series

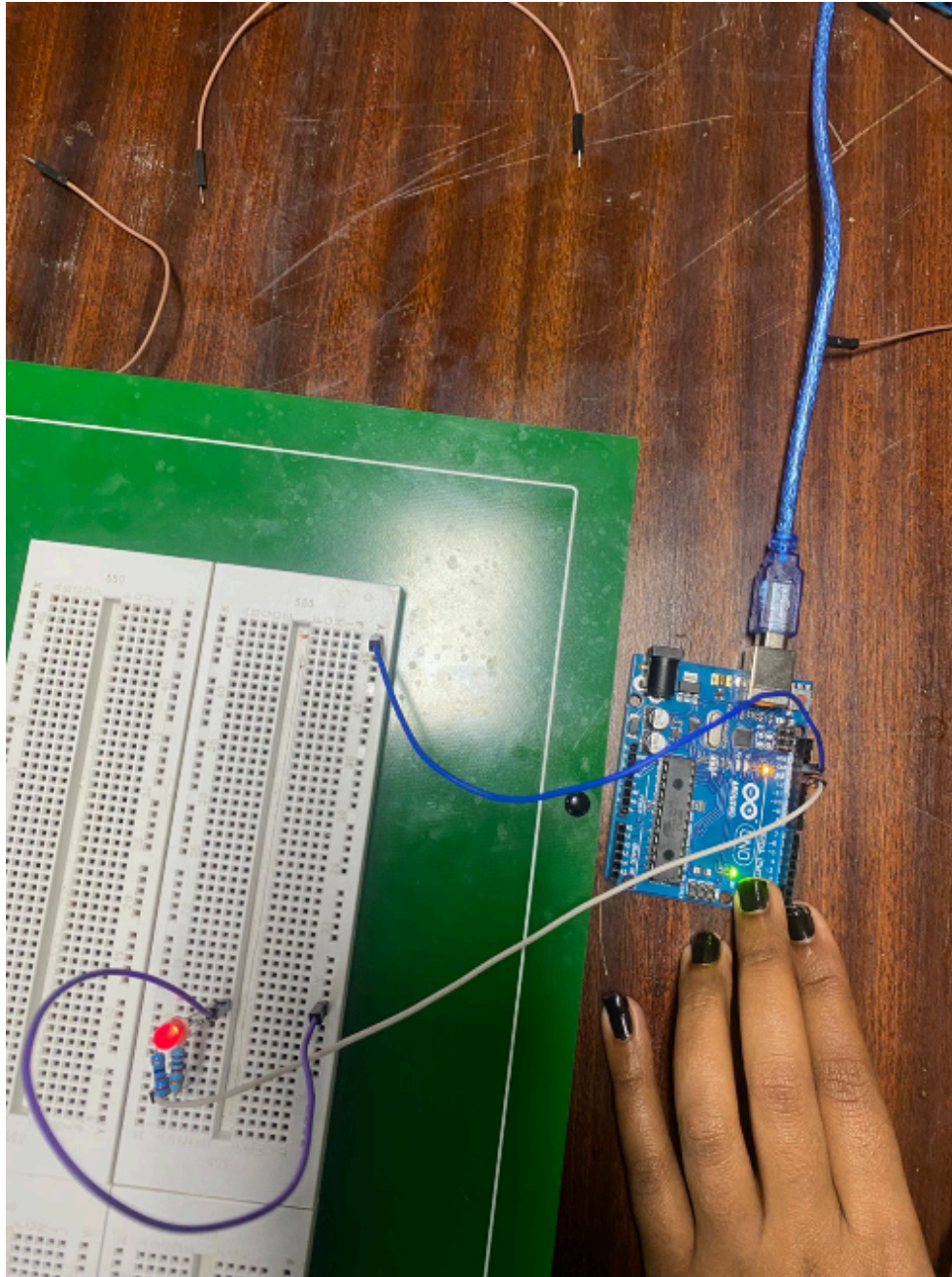

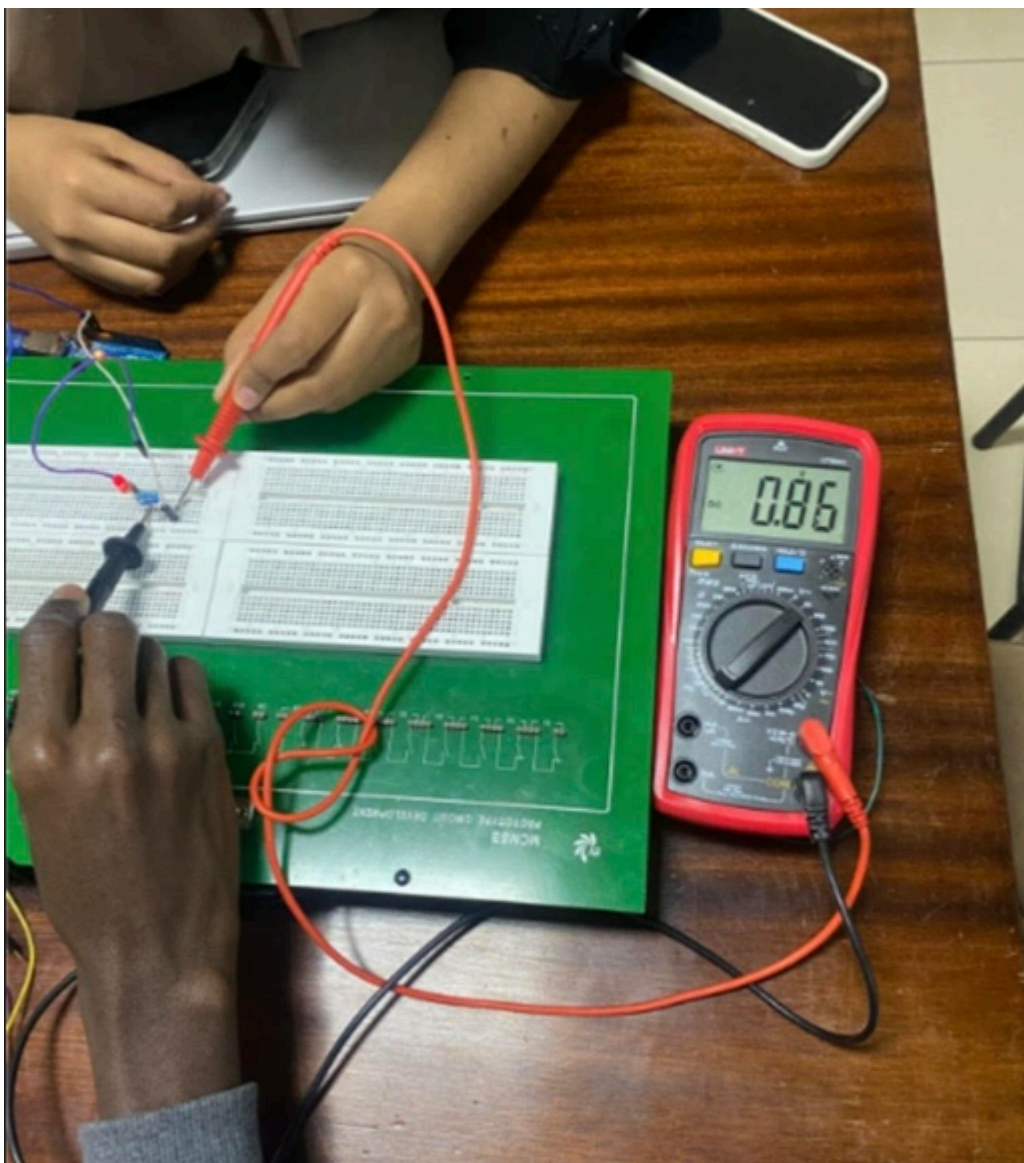Question 2 - Code

```
void setup() {  
  pinMode(8, OUTPUT);  
}  
  
void loop() {  
  digitalWrite(8, HIGH); // LED on  
  delay(1000);  
  digitalWrite(8, LOW); // LED off  
  delay(1000);  
}
```




Voltage = 0.86V.

Experiment 4

Question 1 – Parallel Resistor Circuit

Figure 9: Physical circuit — resistors connected in parallel

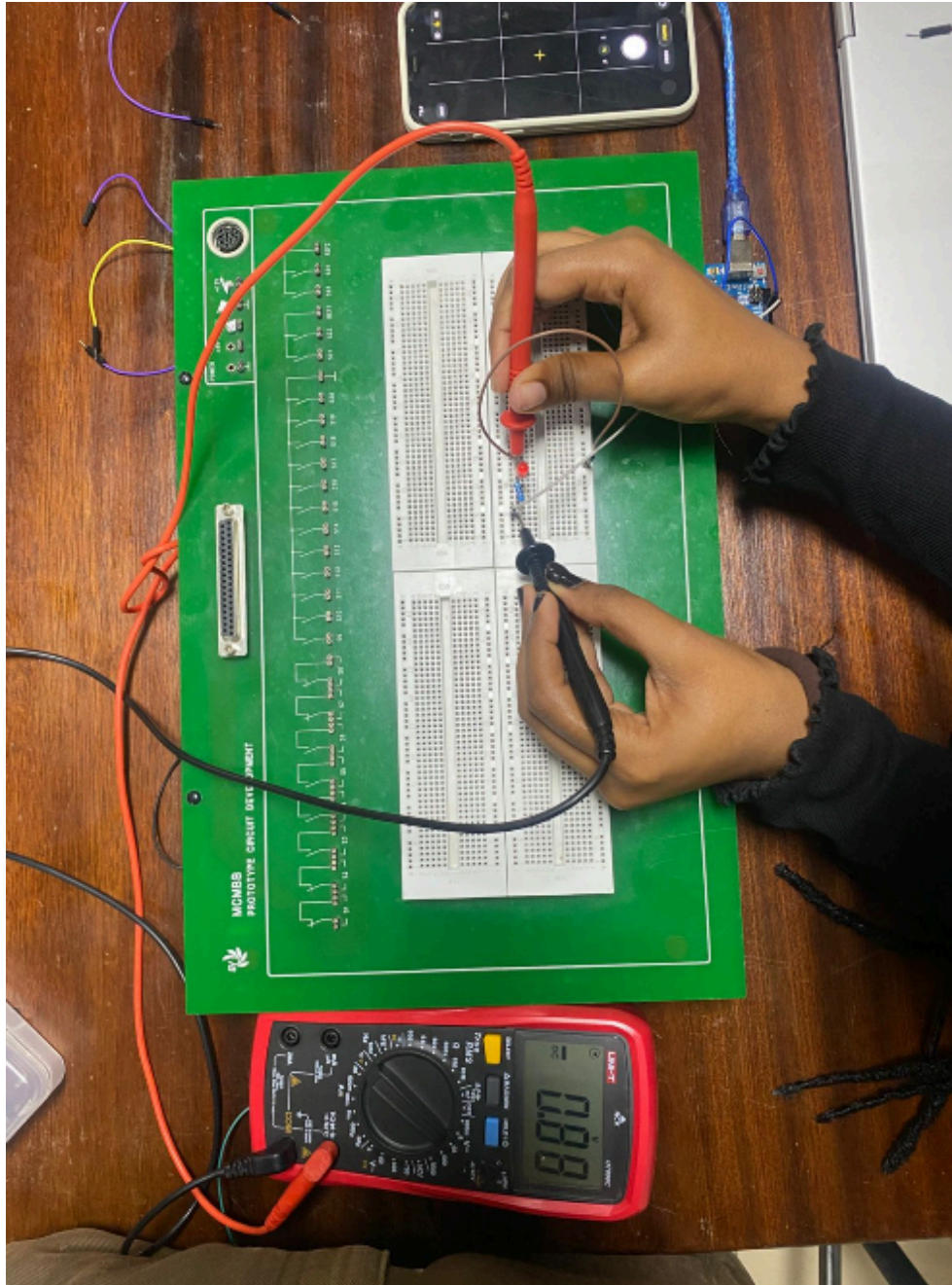

Question 2 - Code

```
void setup() {  
    pinMode(6, OUTPUT);  
}  
  
void loop() {  
    digitalWrite(6, HIGH); // LED on  
    delay(1000);  
    digitalWrite(6, LOW);  // LED off  
    delay(1000);  
}
```

Voltage = **0.88V**.

Group Member Photo.

